
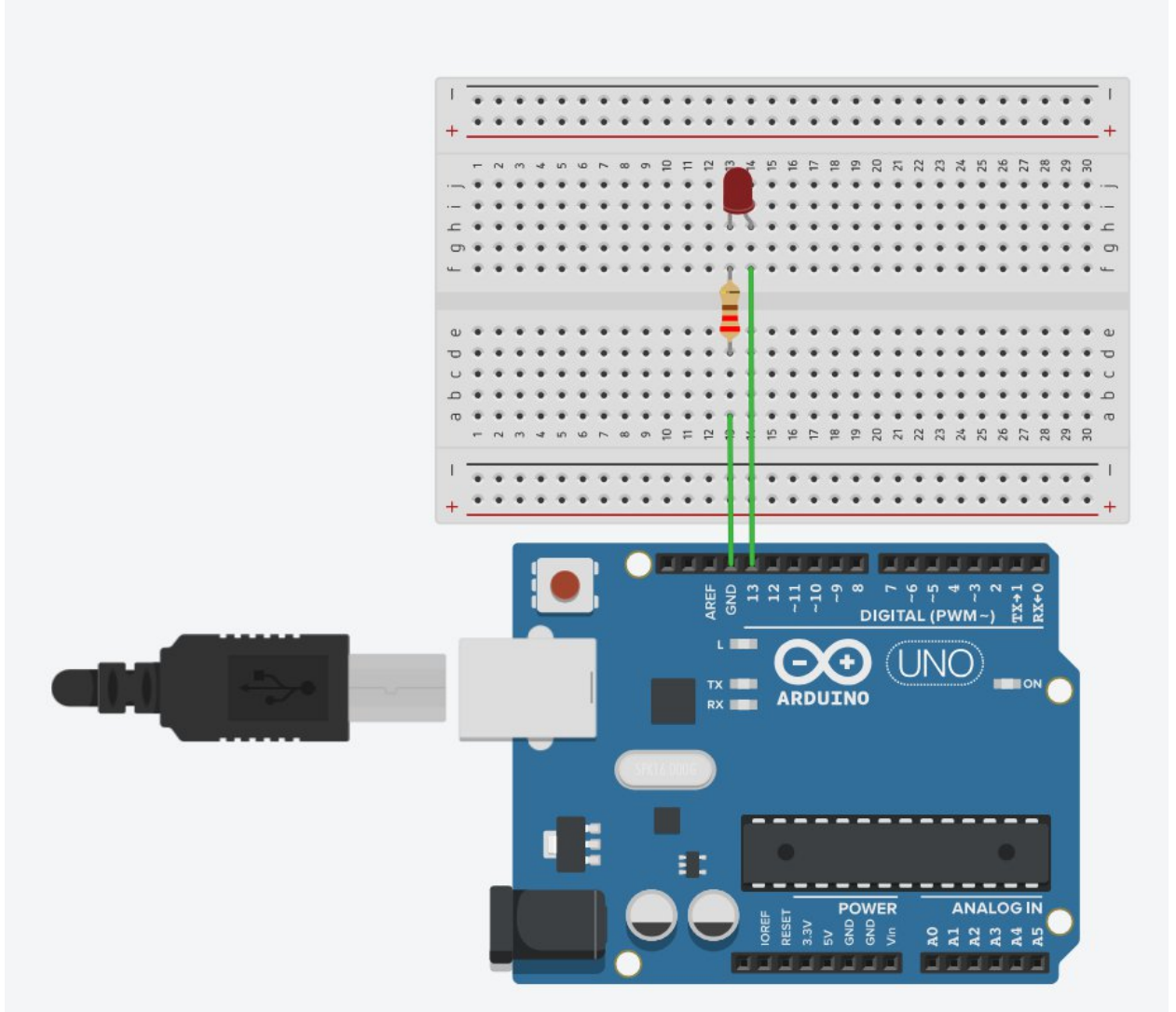


Blink di un LED

1. Circuito

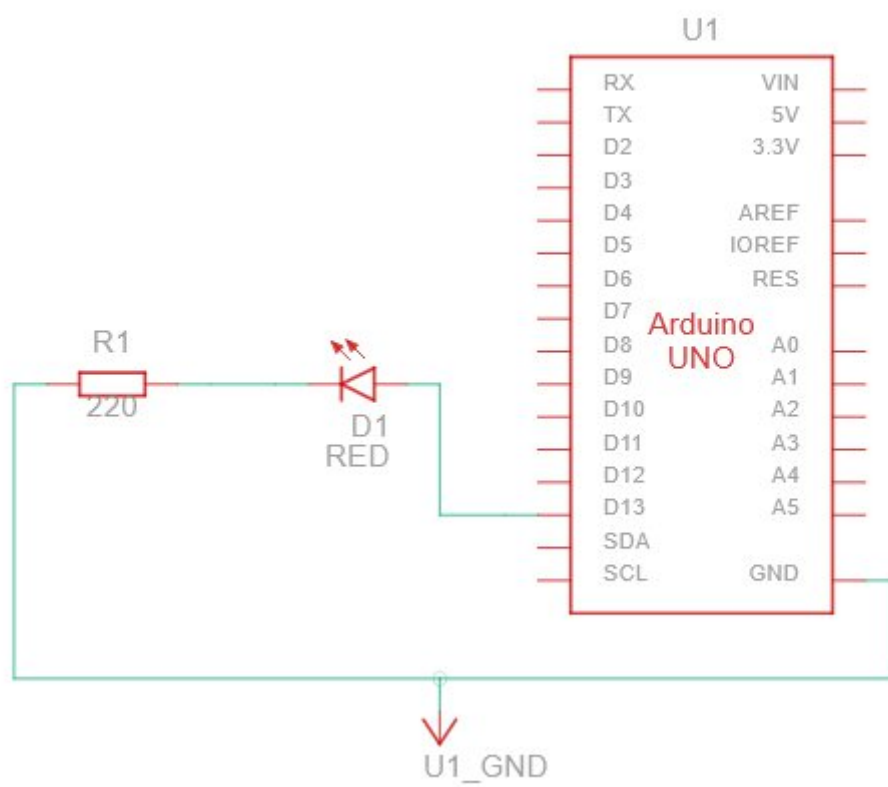

2. Schema elettrico



3. Componenti

Nome	Quantità	Componente
U1	1	Arduino Uno R3
D1	1	Rosso LED
R1	1	220 Ω Resistenza

4. Sketch

```
void setup()

{
  pinMode(13, OUTPUT);
}

void loop()

{
  digitalWrite(13, HIGH);
  delay(1000); // Wait for 1000 millisecond(s)
  digitalWrite(13, LOW);
  delay(1000); // Wait for 1000 millisecond(s)
}
```

5. LINK:

Tinkercad: <https://www.tinkercad.com/things/a08ZbnBwkNg-blink-di-un-led?sharecode=tLdstL7132dgewFNacHsuTJWMKqOaHureAHgAHkF1QY>

Video Tutorial: <https://youtu.be/QSM3sEQxKKw>